



Department of Electrical Engineering

Faculty Member: _____

Dated: _____

Semester: _____

Section: _____

Group No.: _____

EE-221: Digital Logic Design

Lab 08: Magnitude Comparator

Name	Reg. No	PLO4/CLO4	PLO4/CLO4	PLO5/CLO5	PLO8/CLO6	PLO9/CLO7	
		Viva / Lab Performance	Analysis of data in Lab Report	Modern Tool Usage	Ethics and Safety	Individual and Team Work	Total marks Obtained
		5 Marks	5 Marks	5 Marks	5 Marks	5 Marks	25 Marks
AILYA ZAINAB	523506						
IMAN NAEEM	525378						
LAIBA NASIR	510419						
LUQMAN SHEHZAD	507599						



Lab 8: Magnitude Comparator

This Lab Activity has been designed to familiarize students with design and working of combinational circuits using basic logic gates.

Objectives:

- ✓ Design and Implementation of 2-bit magnitude comparator using classical design method learned in the class.
- ✓ Design of a 4-bit magnitude comparator using a 4-bit adder IC and logic gates
- ✓ Verification of 4 bit comparator IC
- ✓ Dataflow modeling in Verilog HDL

Lab Instructions

- ✓ This lab activity comprises three parts, namely Pre-lab, Lab tasks, and Post-Lab Viva session.
- ✓ The lab report will be uploaded on LMS three days before scheduled lab date. The students will get hard copy of lab report, complete the Pre-lab task before coming to the lab and deposit it with teacher/lab engineer for necessary evaluation.
- ✓ The students will start lab task and demonstrate design steps separately for step-wise evaluation(course instructor/lab engineer will sign each step after ascertaining functional verification)
- ✓ Remember that a neat logic diagram with pins numbered coupled with nicely patched circuit will simplify trouble-shooting process.
- ✓ After the lab, students are expected to unwire the circuit and deposit back components before leaving.
- ✓ The students will complete lab task and submit complete report to Lab Engineer before leaving lab.
- ✓ There are related questions at the end of this activity. Give complete answers.




Pre-Lab Tasks (2)

1. What do you mean by a comparator circuit? Draw the truth table for a 1 bit magnitude comparator. The comparator has 2 inputs (A and B) and 3 outputs E, L and G for (A=B), (A<B) and (A>B) respectively. For example, one combination is filled in below example, for your guidance.


A digital comparator or magnitude comparator is a hardware electronic device that takes two numbers as input in binary form and determines whether one number is greater than, less than or equal to the other number.

A	B	E (A=B)	G (A>B)	L (A<B)
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	1	0	0

 
2. Simplify the functions E, G and L and give their Logic diagrams.



Function	Expression
E	$A'B' + AB$
L	$A'B$
G	AB'

 

 3. Design a 2-bit magnitude comparator. The Block diagram is shown below.




a) List the truth table.

Inputs				Outputs		
A1	A0	B1	B0	L (A<B)	E (A=B)	G (A>B)
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1




1	1	1	1	0	1	0
---	---	---	---	---	---	---

 b) Find expressions for the functions E, G and L using k maps.



Simplified expressions:


Function	Expression	Simplified
E	$A_1'A_0'B_1'B_0' + A_1'A_0B_1'B_0 + A_1A_0B_1B_0 + A_1A_0'B_1B_0'$	$(A_1 \odot B_1)(A_0 \odot B_0)$
L	$A_1'B_1 + A_0'B_1B_0 + A_1'A_0'B_0$	N/A
G	$A_1B_1' + A_0B_1'B_0' + A_1A_0B_0'$	N/A


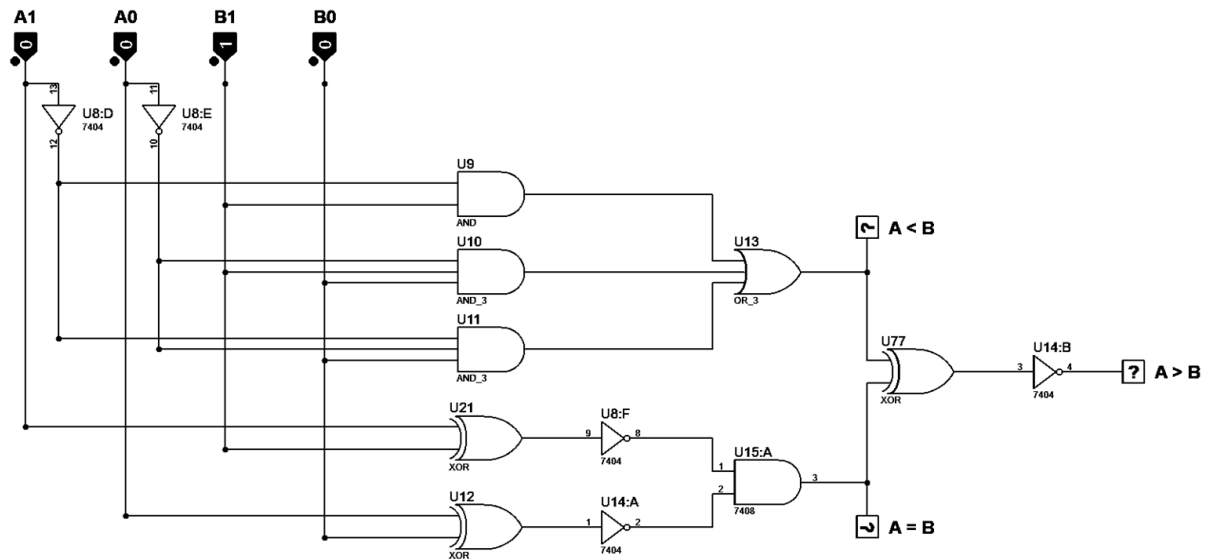




Lab Tasks



1. Implement the 2-bit Comparator circuit you arrived in your Pre-lab Task in Proteus and hardware. (4)

Proteus:

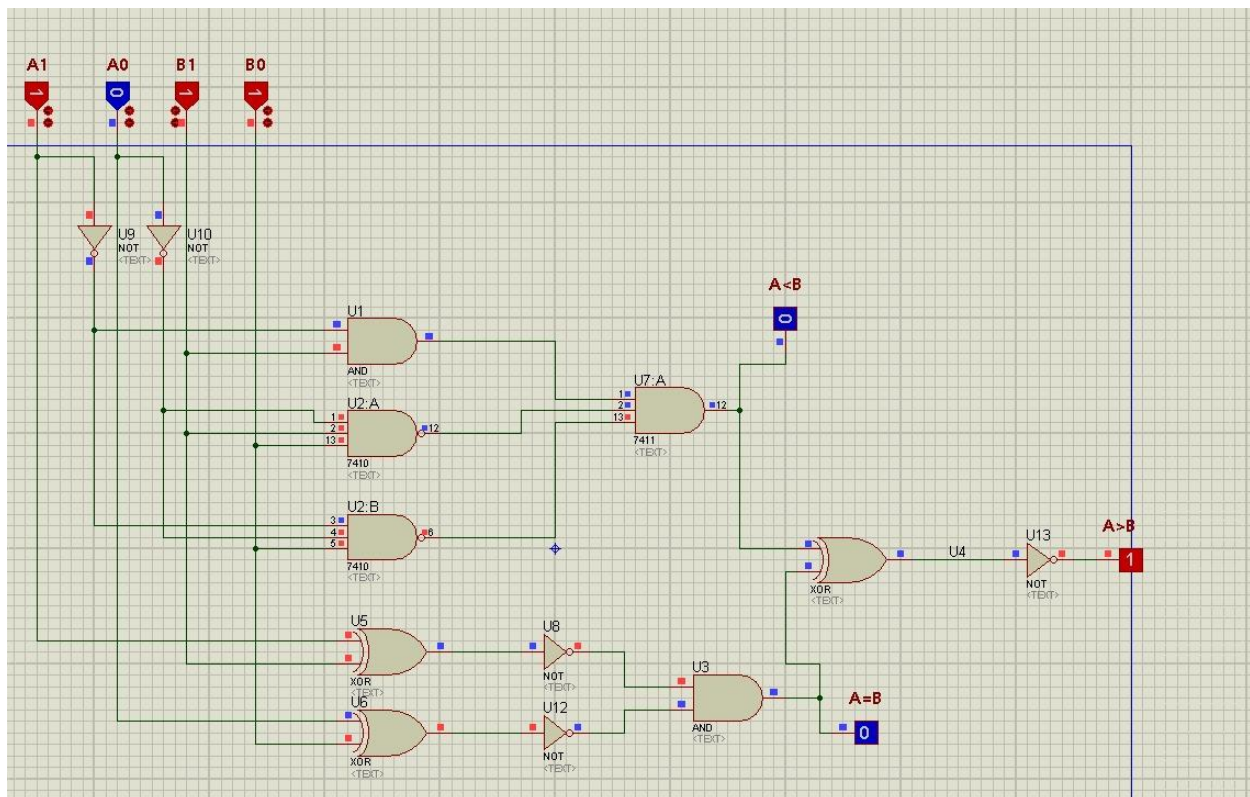

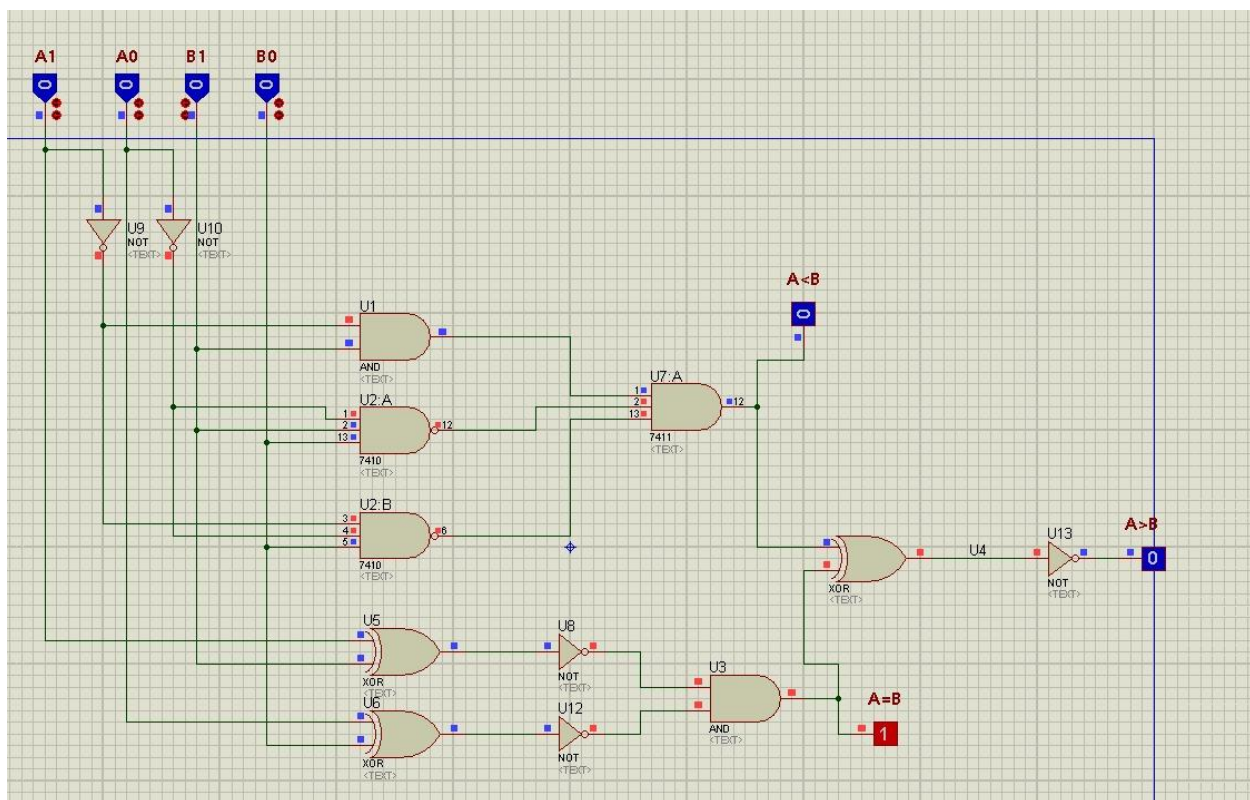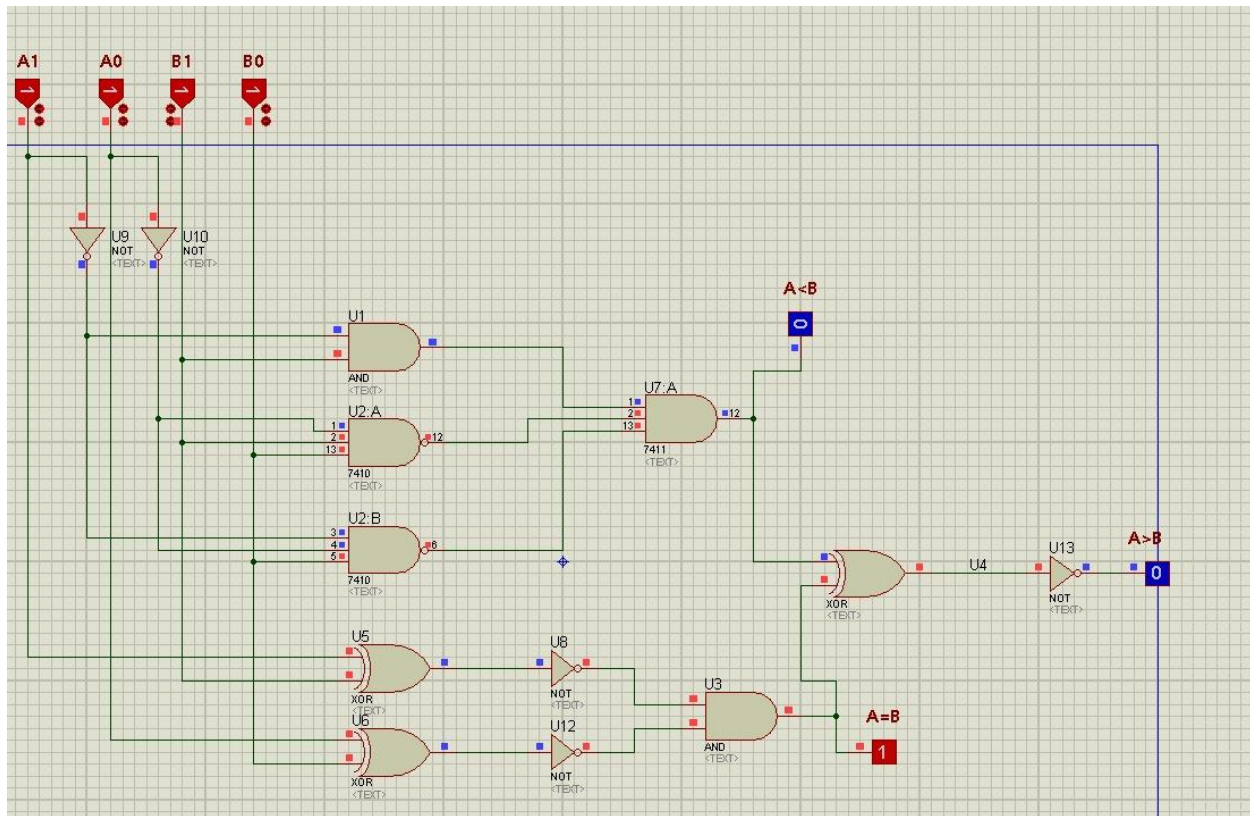

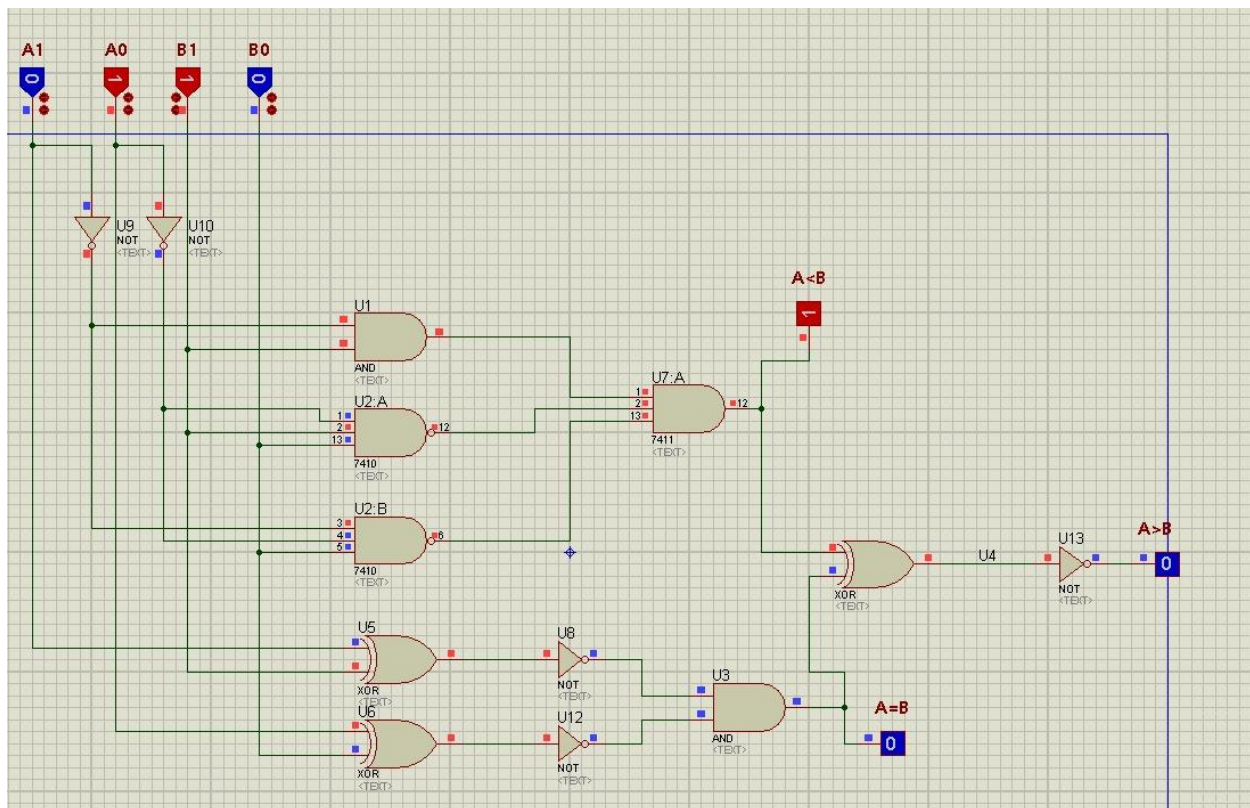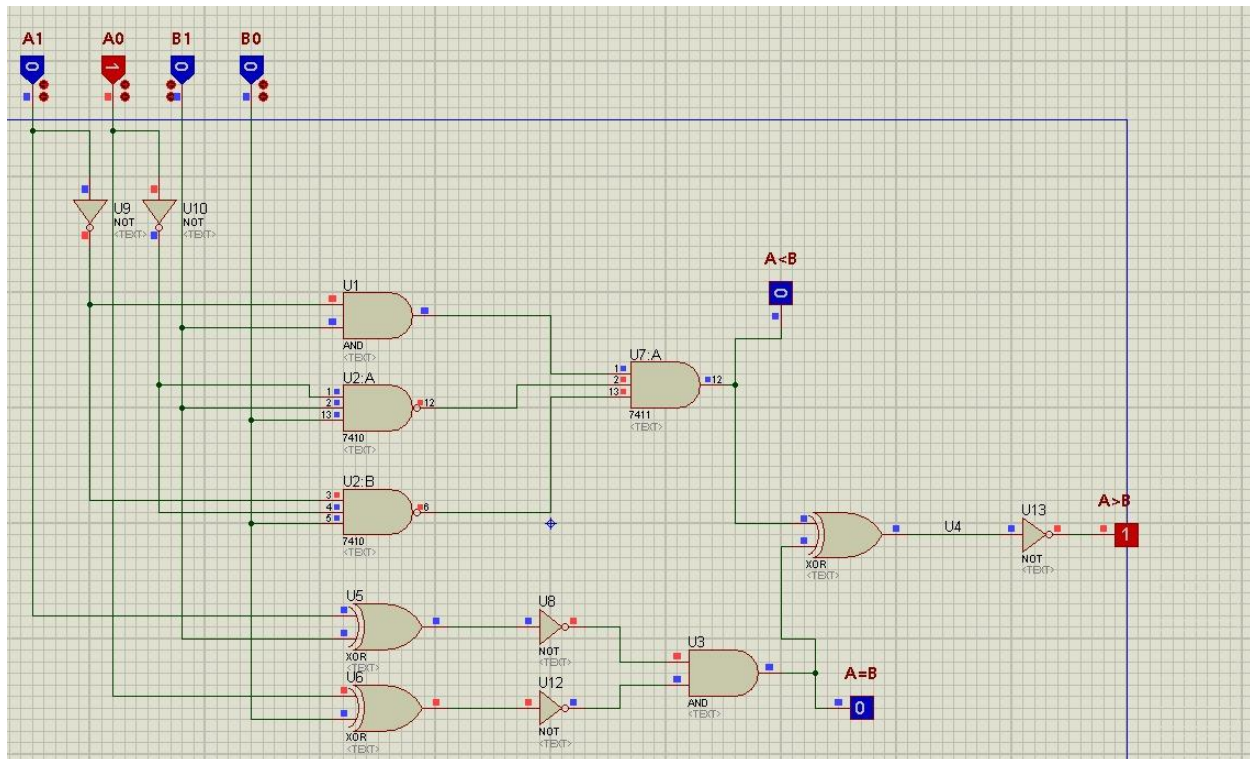


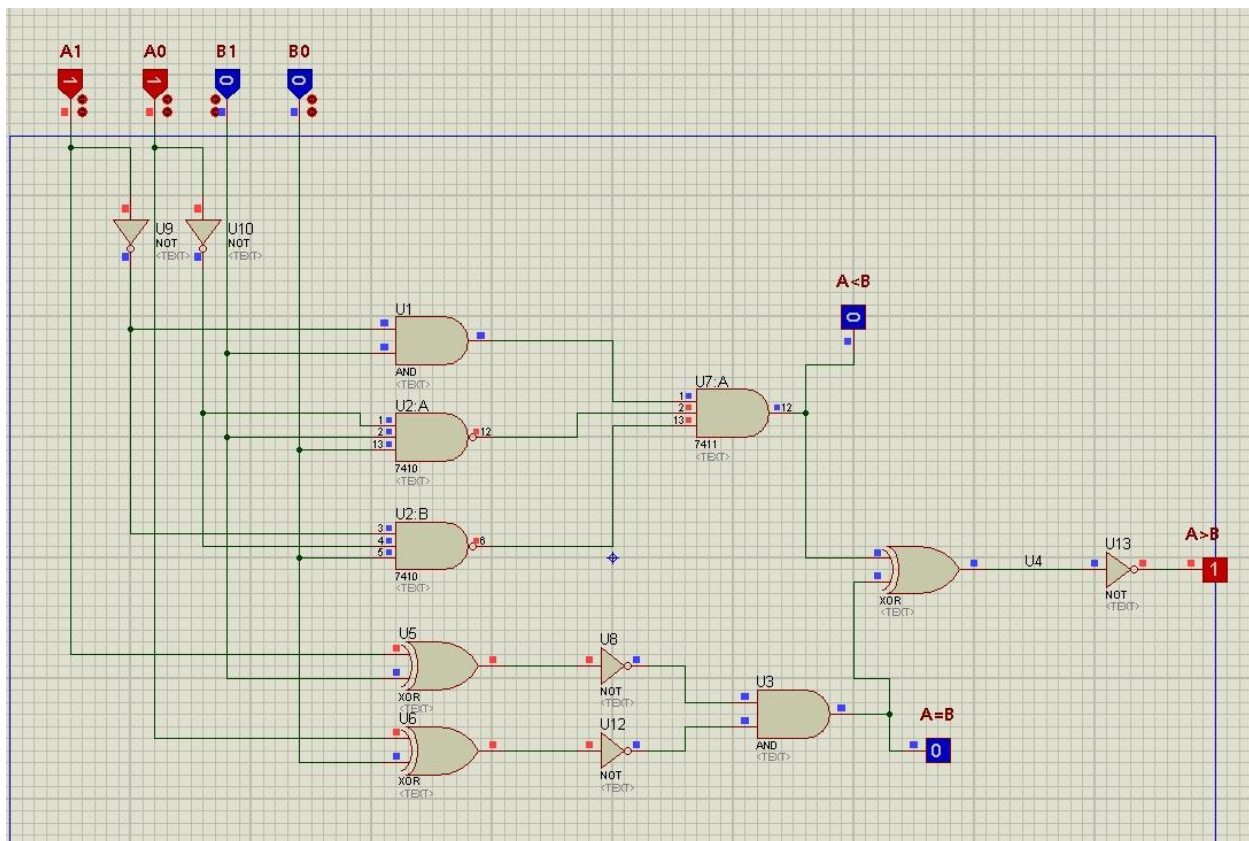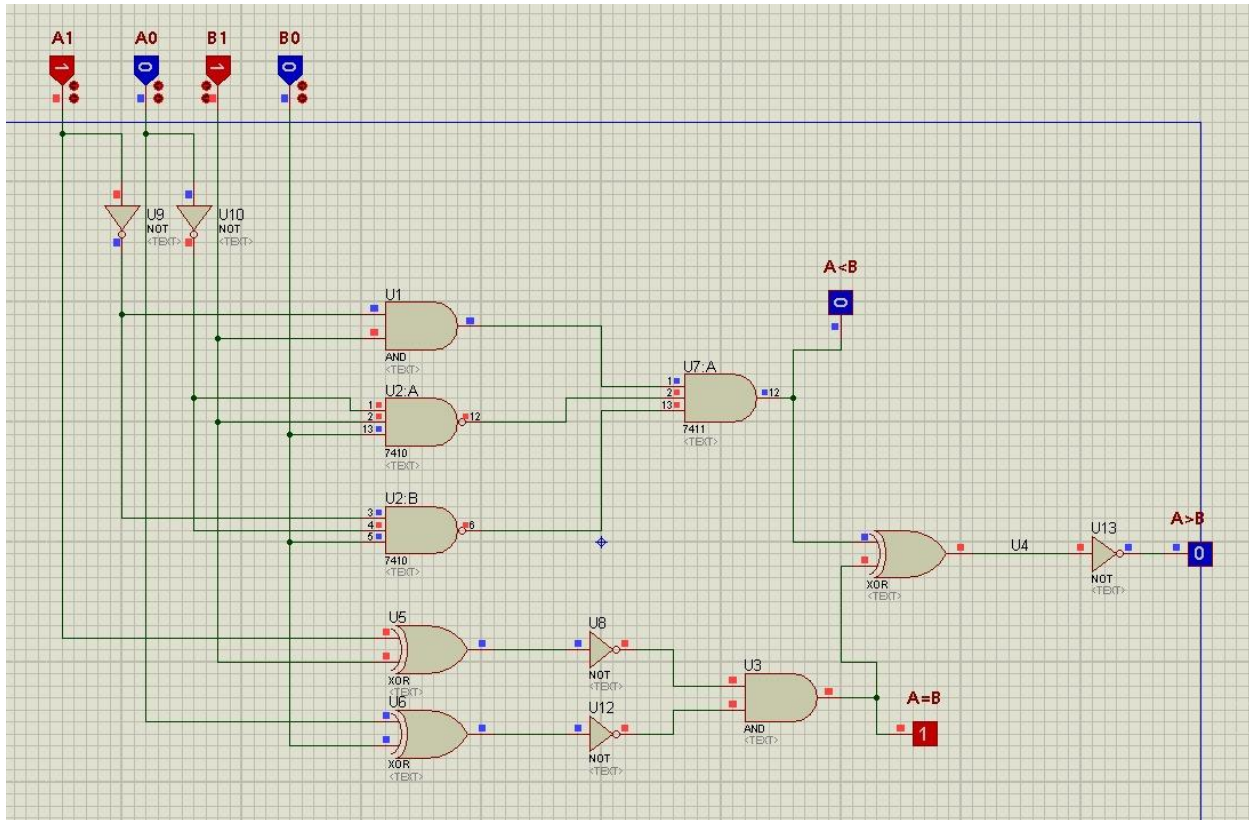



Hardware:



 








2. Write Verilog code of 2 bit comparator using dataflow modeling. (2)




```
1 module comparator(e, g, l, a1, a0, b1, b0);
2
3     input a1, a0, b1, b0;
4     output e, g, l;
5
6     assign e = (a0 ^~ b0) & (a1 ^~ b1);
7     assign g = (a1 & ~b1) | (a0 & ~b1 & ~b0) | (a1 & a0 & ~b0);
8     assign l = (~a1 & b1) | (~a0 & b1 & b0) | (~a1 & ~a0 & b0);
9
10 endmodule
11
12 module testbench80;
13
14     reg A1, A0, B1, B0;
15     wire E, G, L;
16
17     comparator t1(E, G, L, A1, A0, B1, B0);
18
19     initial begin
20         #100 A1 = 0; A0 = 0; B1 = 0; B0 = 0;
21         #100 A1 = 0; A0 = 0; B1 = 0; B0 = 1;
22         #100 A1 = 0; A0 = 0; B1 = 1; B0 = 0;
23         #100 A1 = 0; A0 = 0; B1 = 1; B0 = 1;
24         #100 A1 = 0; A0 = 1; B1 = 0; B0 = 0;
25         #100 A1 = 0; A0 = 1; B1 = 0; B0 = 1;
26         #100 A1 = 0; A0 = 1; B1 = 1; B0 = 0;
27         #100 A1 = 0; A0 = 1; B1 = 1; B0 = 1;
28         #100 A1 = 1; A0 = 0; B1 = 0; B0 = 0;
29         #100 A1 = 1; A0 = 0; B1 = 0; B0 = 1;
30         #100 A1 = 1; A0 = 0; B1 = 1; B0 = 0;
31         #100 A1 = 1; A0 = 0; B1 = 1; B0 = 1;
32         #100 A1 = 1; A0 = 1; B1 = 0; B0 = 0;
33         #100 A1 = 1; A0 = 1; B1 = 0; B0 = 1;
34         #100 A1 = 1; A0 = 1; B1 = 1; B0 = 0;
35         #100 A1 = 1; A0 = 1; B1 = 1; B0 = 1;
36     end
37
38 endmodule
39
```

Wave form:

 



2.

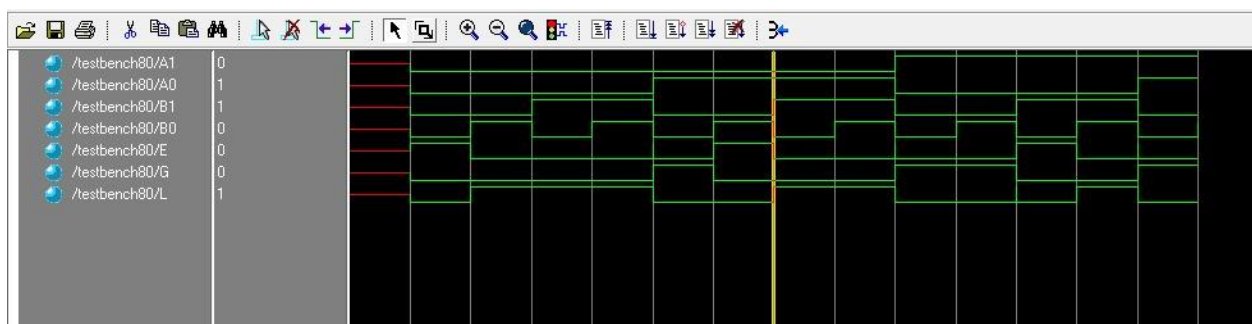




3. Simulate the 4-bit magnitude comparator IC (7485) in Proteus. Give its function table, Pin Layout and show its Proteus. (2)

Proteus:

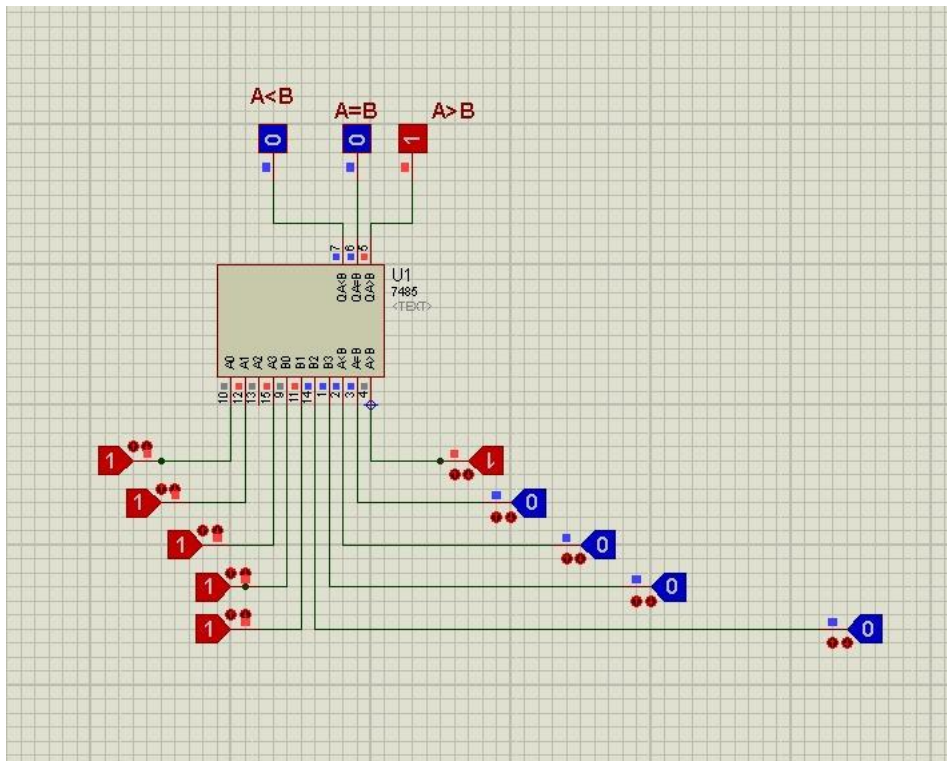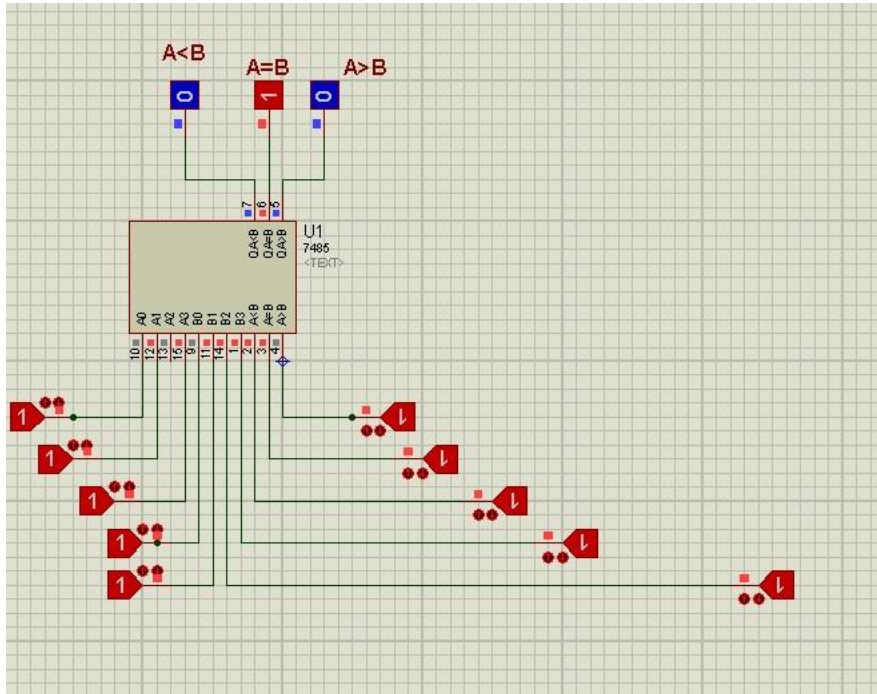



Pin layout:

 

Pin Layout of 7485

Function Table:

A3	A2	A1	A0	B3	B2	B1	B0	E (A=B)	G (A>B)	L (A<B)
0	0	0	0	0	0	0	0	1	0	0
0	0	0	1	0	0	1	1	0	1	0
0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	1	0	0	1
0	1	0	0	0	1	0	0	1	0	0
0	1	0	1	0	0	1	1	0	0	1
0	1	1	0	0	1	0	1	0	0	1
0	1	1	1	1	0	0	1	0	1	0
1	0	0	0	1	0	0	0	1	0	0
1	0	0	1	0	1	1	1	0	0	1
1	0	1	0	1	0	1	1	0	1	0
1	0	1	1	1	0	1	0	0	0	1
1	1	0	0	1	1	0	0	1	0	0
1	1	0	1	1	1	1	0	0	1	0
1	1	1	0	1	1	1	1	0	1	0
1	1	1	1	1	1	1	1	1	0	0