



**Department of Electrical Engineering**

Faculty Member: Miss Rafia

Dated: 11-3-25

Semester: 2nd

Section: ds-2a

**EE-241: Digital Logic Design**

Group No.:

**Lab 07: Design a display system of a rolling dice**

Name	Reg. No	PLO4/CLO4	PLO4/CLO4	PLO5/CLO5	PLO8/CLO6	PLO9/CLO7	Total marks Obtained
		Viva / Lab Performance	Analysis of data in Lab Report	Modern Tool Usage	Ethics and Safety	Individual and Team Work	
		5 Marks	5 Marks	5 Marks	5 Marks	5 Marks	25 Marks
AILYA ZAINAB	523506						
IMAN NAEEM	525378						
LAIBA NASIR	510419						
LUQMAN SHEHZAD	507599						




**Lab7: Design a system that display from 1 to 6. It displays the result on a dice. The dice has seven lights**

This Lab Activity has been designed to practice the use of basic gates for designing a system


- Simplification of Combinational Circuits
- Design and Implementation of a design a system to display dice values.
- Values-Segment Decoder for Selected Digit Display
- There are related questions at the end of this activity. Give complete answers. Use diagrams if needed for clarity.

 **PreLab Task (2 marks)**

Design a system that display from 1 to 6 (ONLY)i.e. it shows no output in case of illegal input like 0 and 7. It displays the result on a dice. The dice has seven LEDs a,b,c,d,e,f,g, placed in H shape pattern as shown on the diagram below



 A 1 for each segment ( a, b, c, d, e, f, g) indicates that it is lit (on); and a 0 that it is off. The arrangement is the six numbers on a dice are shown below; where the darkened circles depicts LED is ON. **(Make sure to switch off all the lights in Don't care case)**



- Design a driver that produces the seven LED (a, b, c, d, e, f, g) to drive the display.
1. Complete the following table. **(Make sure to switch off all the lights in Don't care case)** (First 3 inputs are filled for guidance)



Inputs (Binary)				Outputs (7 LEDs on Dice Display)						
#m	A	B	C	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1	0	0	0
2	0	1	0	1	0	0	0	0	0	1
3	0	1	1	1	0	0	1	0	0	1
4	1	0	0	1	0	1	0	1	0	1
5	1	0	1	1	0	1	1	1	0	1
6	1	1	0	1	1	1	0	1	1	1
7	1	1	1	0	1	0	0	0	0	0

- Write minimum possible functions to realize outputs (Either using k-mapping/ or minimization of Boolean function) (**Make sure to switch off all the lights in Don't care case**). Show and get verified the minimized Boolean Function expressions to Lab Engineer before implementation.

Hint: You will get 7 output expressions. Output expression for 'a' and 'g' will be same. Output expression for 'b', and 'f' will be same. Output expression for 'c', and 'e' will be same.



**For a and g**

A \ BC	00		01		11		10	
	0	1	0	1	0	1	0	1
0	0	0	1	1	0	0	1	1
1	1	1	0	0	1	1	0	0

**For b and f**

A \ BC	00		01		11		10	
	0	1	0	1	0	1	0	1
0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	1	1

**For c and e**

A \ BC	00		01		11		10	
	0	1	0	1	0	1	0	1
0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	1	0	0

**For d**


A \ BC	00		01		11		10	
	0	1	0	1	0	1	0	1
0	0	0	1	1	0	0	0	0
1	0	0	1	1	0	0	0	0

**Simplified Expressions**


Variable		Expression
a	g	$(A \oplus B) + BC'$
b	f	$A(BC')$
c	e	$A(B'+C')$
d	-	$C(A'+B')$



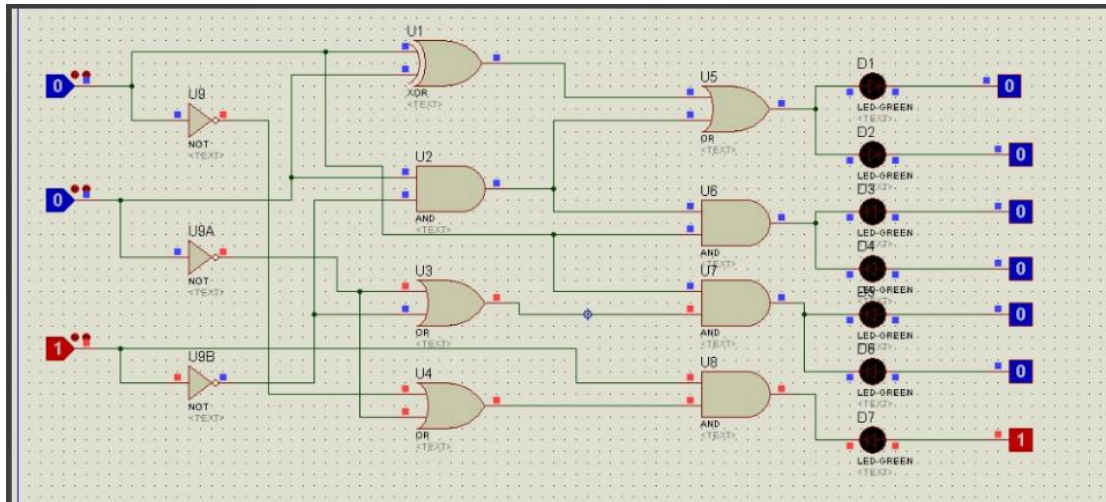- Draw the complete logic circuit diagram of the system from simplified equations (Proteus)



DICE FORM OUTPUT:

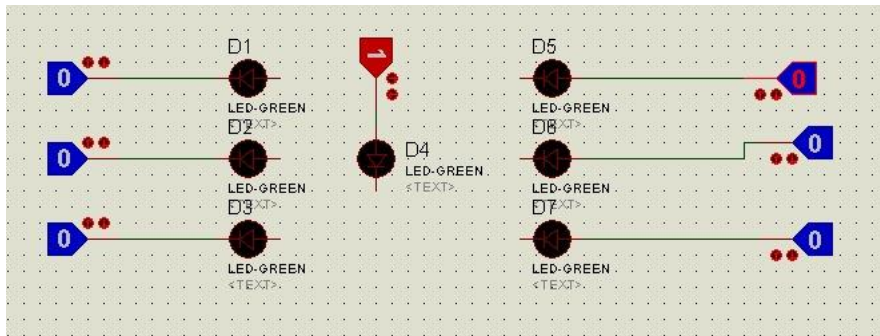



## Lab Task 1 (5 marks)

- Implement the designed logic circuit on hardware. Utilize your creativity to make the Dice display **model**


Inputs (Binary)				Outputs (7 LEDs on Dice Display)						
#m	A	B	C	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1	0	0	0
2	0	1	0	1	0	0	0	0	0	1
3	0	1	1	1	0	0	1	0	0	1
4	1	0	0	1	0	1	0	1	0	1
5	1	0	1	1	0	1	1	1	0	1
6	1	1	0	1	1	1	0	1	1	1
7	1	1	1	0	1	0	0	0	0	0

### Hardware Implementation






 
# National University of Sciences and Technology (NUST) School of Electrical Engineering and Computer Science



## PROTEUS:

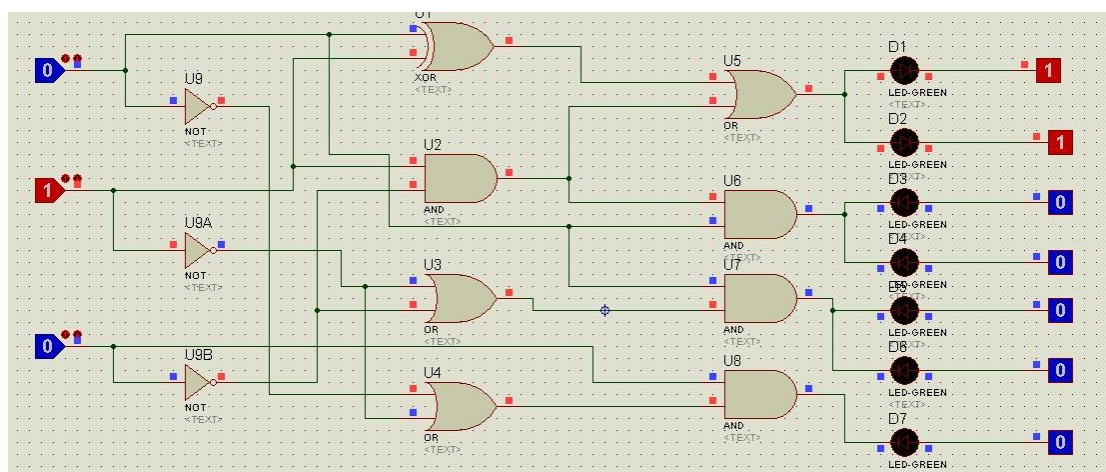



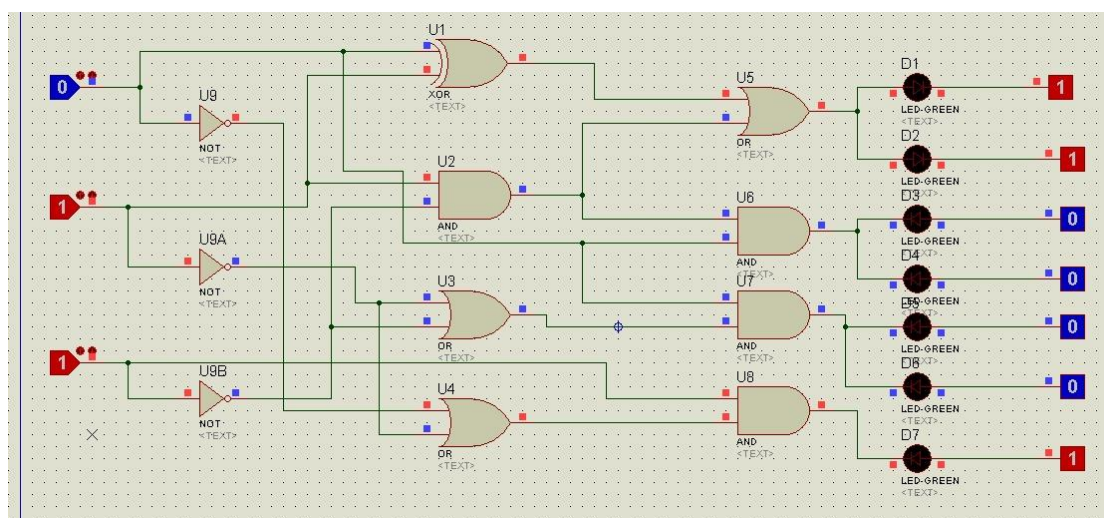







# National University of Sciences and Technology (NUST)
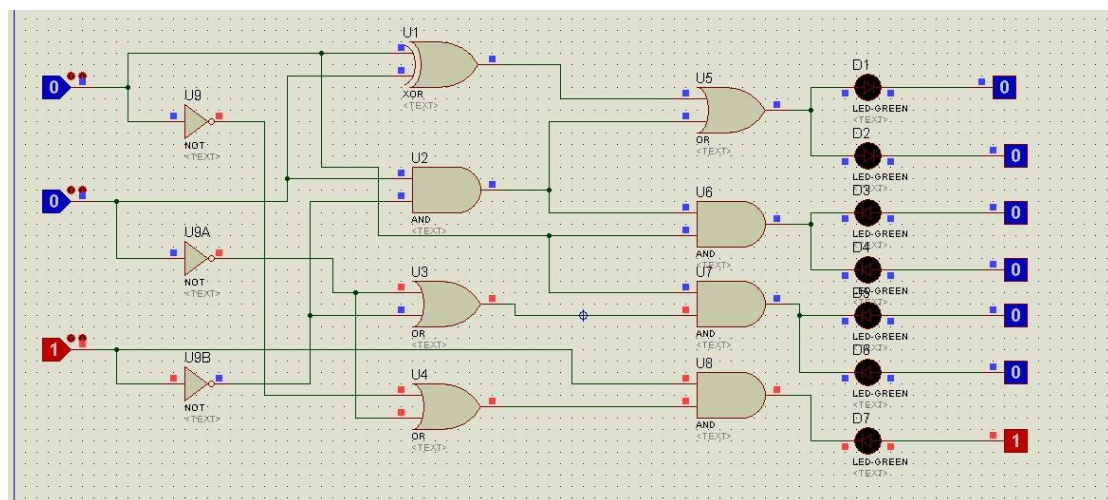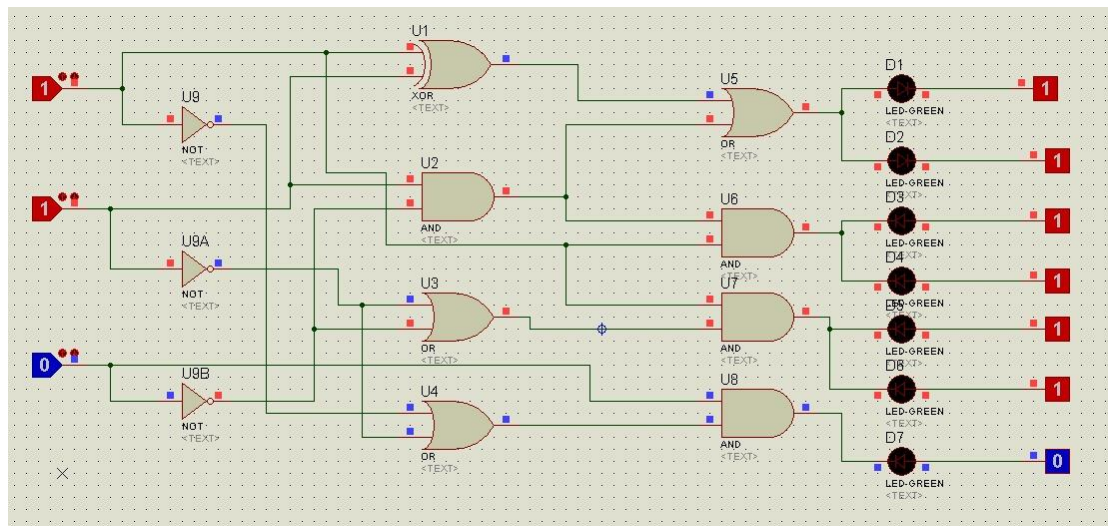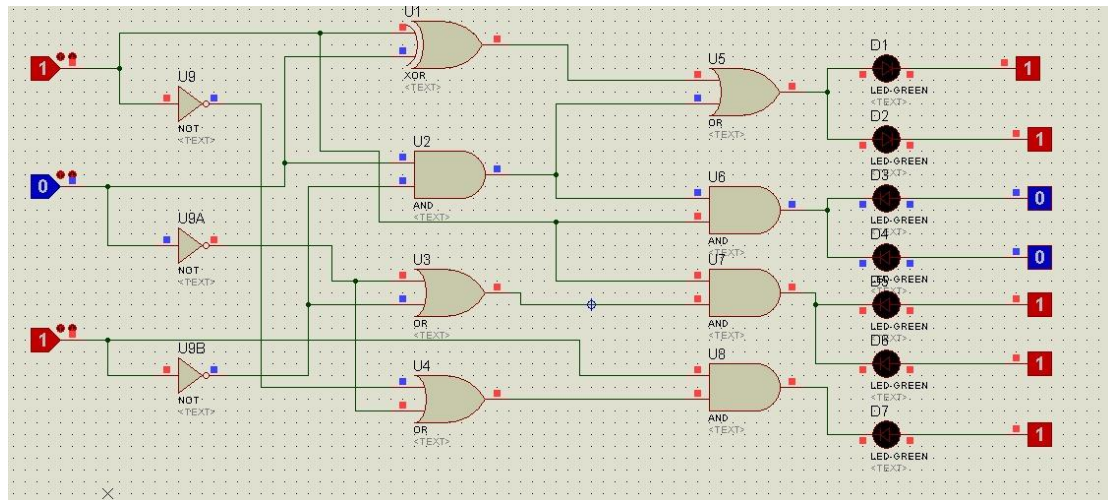
## School of Electrical Engineering and Computer Science



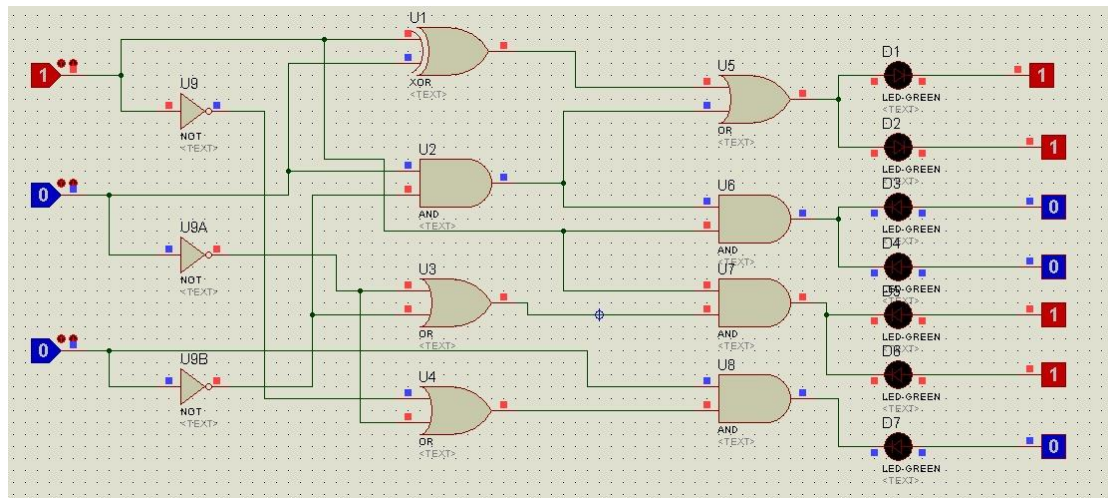

## Lab Task 2 (3 marks)

- Write Verilog code to realize the design using dataflow model. Design also test bench to check the valid outputs. Include all the snap shots and Verilog code in the report.

### CODE:

```
module task1(a, b, c, d, e, f, g, A, B, C);  
    input A, B, C;  
    output a, b, c, d, e, f, g;  
  
    assign a = (~A & B) | (A & ~B) | (B & ~C);  
    assign g = (~A & B) | (A & ~B) | (B & ~C);  
  
    assign b = A & (B & ~C);  
    assign f = A & (B & ~C);  
  
    assign c = A & (~B | ~C);  
    assign e = A & (~B | ~C);  
  
    assign d = C & (~A | ~B);  
endmodule  
  
module testbench;  
  
    reg A, B, C;  
  
    wire a, b, c, d, e, f, g;
```



```
task1 t1(a, b, c, d, e, f, g, A, B, C);
```

```
initial
```

```
begin
```

```
#100 A = 0; B = 0; C = 0;
```

```
#100 A = 0; B = 0; C = 1;
```

```
#100 A = 0; B = 1; C = 0;
```

```
#100 A = 0; B = 1; C = 1;
```

```
#100 A = 1; B = 0; C = 0;
```

```
#100 A = 1; B = 0; C = 1;
```

```
#100 A = 1; B = 1; C = 0;
```

```
#100 A = 1; B = 1; C = 1;
```

```
end
```

```
Endmodule
```

### WAVE FORM:



### Observations/Comments:

In this lab we implemented the logic to design a display system of a rolling dice using:

1. Basic gates (AND, NOT and OR)
2. Using XOR



## **National University of Sciences and Technology (NUST)**

### **School of Electrical Engineering and Computer Science**

We implemented the LEDs (placed in an H - shape) at the receiver end of the circuit and wrote the Verilog code for the circuit and verified the outputs.